

Computer Science at The Dragon Academy
Assignment III
Review of Propositional Logic, Logic Gates & Circuits
Due date: Wed. Oct. 31st 2018

October 26, 2018

50% questions and 50% problems.

1 Exercises

1. (KtiCa) Given $p : x + y = 5$ and $q : x \cdot y \geq 6$, translate to English/math the following expressions (use math for expressing identities or inequalities):
 - (a) $\neg q \rightarrow \neg p$
 - (b) $p \oplus q$
 - (c) $p \vee q$
 - (d) $\neg q \rightarrow (p \vee \neg p)$
2. (KtiCa) Identify p and q from $p \wedge q \equiv \text{"It's raining and cold"}$ and find a natural translation to English of the following sentences:
 - (a) $\neg(p \wedge q)$
 - (b) $\neg q \rightarrow (p \vee \neg p)$
3. (KtiCa) Prove that $((p \rightarrow q) \wedge (q \rightarrow r)) \rightarrow (p \rightarrow r)$
4. (KtiCa) Prove that $[(a \rightarrow (b \rightarrow c)) \wedge (a \wedge b)] \rightarrow c$
5. (KtiCa) Simplify and determine whether each of the following sentences is (a) contingent, (b) contradictory or (c) tautological:
 - (a) $(p \rightarrow q) \rightarrow \neg q$
 - (b) $p \rightarrow \neg p$
 - (c) $[(p \rightarrow r) \rightarrow (p \wedge q)] \wedge r \wedge \neg q$
6. (KtiCa) Consider a gate consisting in two CNOT gates coupled in series, i.e., the output of the first is fed into the input of the second.
 - (a) Write the truth table of such a gate
 - (b) If we call the top and bottom inputs x, y , respectively, and the top and bottom outputs x', y' , respectively, determine an algebraic expressions for x' and y' in terms of x and y
 - (c) A CNOT gate is reversible. This means we can build a gate, the *inverse gate* of the CNOT, that *undoes* what the CNOT does. What is that gate?

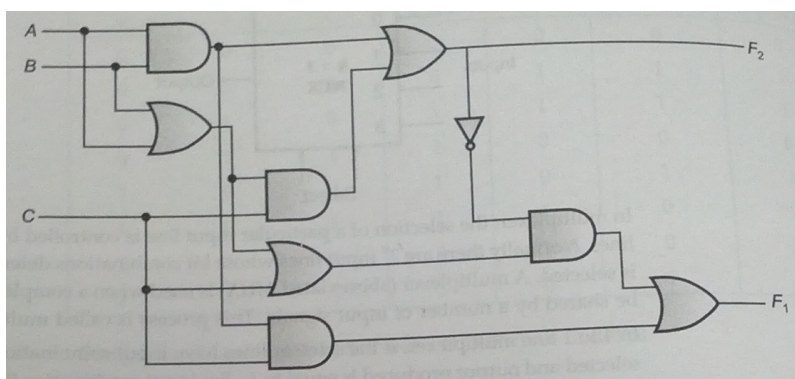


Figure 1: Logic circuit 1

2 Problems

7. (ktiCA) Determine the expressions for F_1 and F_2 as given by the circuit of figure 1 and simplify as much as possible.
8. (kTiCa) Consider the circuit of figure 2 and determine the expressions for a , b , c in the following cases. What function do we obtain in each case?
 - (a) $y = 1$
 - (b) $z = 0$
 - (c) $x = \neg a$ and $y = \neg b$ and $z = 0$

8. (kTICa) Consider the circuit of figure 2 and determine the expressions for a , b , c in the following cases. What function do we obtain in each case?

- $y = 1$
- $z = 0$
- $x = \neg a$ and $y = \neg b$ and $z = 0$

- (b) $z = 0$

- (c) $x = \top a$ and $y = \top b$ and $z = 0$

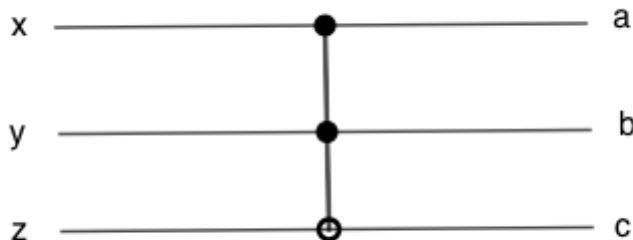


Figure 2: Toffoli gate

9. (kTlca) From your answers to exercise 8), figure out how to write the OR gate using only NOT's and a CNOT.